

CRM08

Rev 1.10

<EC>

<29/01/2021>

CONTINUOUS INTERNAL EVALUATION - I

Dept: FY	Sem / Div: I D,E,F	Sub: Basic Electronics	S Code: 1SELN14
Date: 02/02/2021	Time: 3:00- 4:30pm	Max Marks: 50	Elective: N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
PART A				
1	a Explain the working of PN junction diode under forward and reverse biased conditions.	8	L2	CO1
	b Explain V-I characteristics of photo-diode and its operation.	5	L2	CO1
	c Explain the construction working and characteristics n-channel JFET.	8	L2	CO2
	d For the circuit shown in Fig, find current and voltages in the circuit for $R_L = 450\Omega$. (Assume $V_Z = 4V$)	4	L3	CO1
OR				
2	a what is semiconductor diode? Explain the different equivalent circuits of diode	6	L2	CO1
	b Write a short note on (i) Light emitting diode and (ii) Photo coupler.	6	L1	CO1

c Calculate the output voltage of a summer. Given $R_1=200k\Omega$, $R_2=250k\Omega$, $R_3=500k\Omega$, $R_f=1M\Omega$, $V_1=-2v$, $V_2=-1v$, $V_3=+3v$

4 L2 CO3
5 L2 CO1


PART B

3 a Explain the VI characteristics of SCR.

6 L2 CO2

b Calculate the output Voltage for the circuit shown below

8 L2 CO3

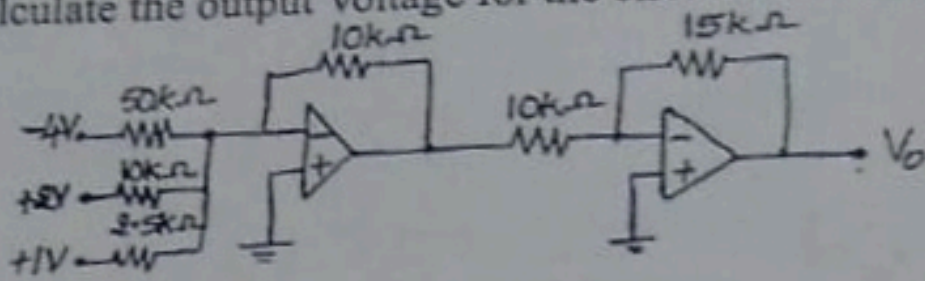

c Design an op-amp circuit to get output voltage of $V_o = -(0.1V_1 + 0.5V_2 + 20V_3)$. Select $R_f = 10k\Omega$

6 L2 CO3

d Explain a simple application of a transistor switch.

5 L2 CO1

OR

4 a Explain the working of SCR using two transistor model


5 L2 CO2

b Explain the operation of op-amp as a non-inverting amplifier with a neat diagram and waveform.

8 L2 CO3

c For an op-amp circuit shown find output voltage V_{o1} and V_{o2}

6 L2 CO3

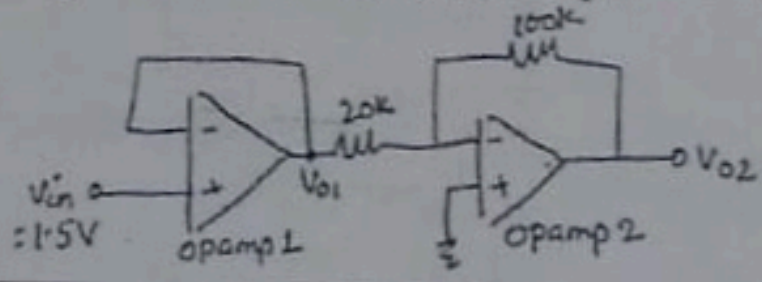

d In a transistor amplifier circuit determine the voltage gain and ac output voltage if $V_b = 100mV$, $R_c = 1k\Omega$ and $r_e' = 50\Omega$.

6 L2 CO

SHRUTHI P R

Prepared by: SHRUTHI P R

HOD